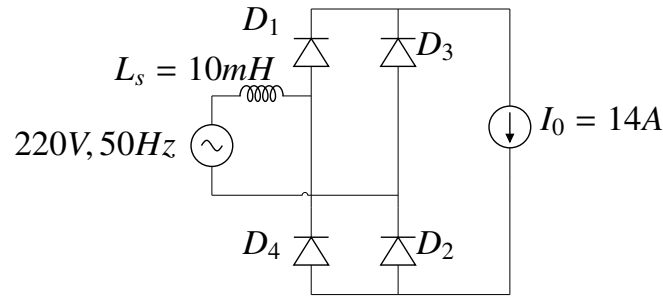



# 2017-EE-53-65

EE24BTECH11001 - ADITYA TRIPATHY

- 1) The figure below shows an uncontrolled diode bridge rectifier supplied from 220V, 50Hz 1-phase ac source. The load draws a constant current  $I_0 = 14A$ . The conduction angle of the diode  $D_1$  in degrees (rounded off to two decimal places) is (2017 – EE)



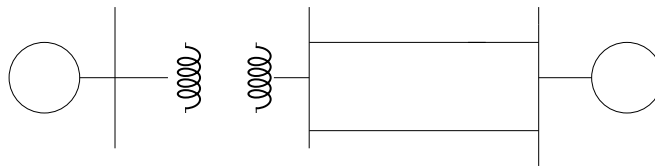- 2) The positive, negative and zero sequence reactances of a wye-connected synchronous generator are  $0.2pu$ ,  $0.2pu$  and  $0.1pu$ , respectively. The generator is on open circuit with terminal voltage of  $1pu$ . The minimum value of the inductive reactance, in  $pu$ , required to be connected between neutral and ground so that the fault current does not exceed  $2.75pu$  is a single line to ground fault occurs at the terminals is (assume fault impedance to be zero). (Give the answer up to one decimal place) (2017 – EE)
- 3) The figure shows the single line diagram of a power system with a double circuit transmission line. The expression for electrical power is  $1.5 \sin \delta$ , where  $\delta$  is the rotor angle. The system is operation at the stable equilibrium point with mechanical power equal to  $1pu$ . If one of the transmission line circuits is removed, the maximum value of  $\delta$ , as the rotor swings is  $P_{max} \sin \delta$ , the value of  $P_{max}$ , in  $pu$  is (Give the answer up to three decimal place) (2017 – EE)



- 4) After Rajendra Chola returned from his voyage to Indonesia, he \_\_\_\_\_ to visit the temple in Thanjavur. (2017 – EE)
- a) was wishing      b) is wishing      c) wished      d) had wished
- 5) Research in the workplace reveals that people work for many reasons \_\_\_\_\_. (2017 – EE)
- a) money beside      b) beside money      c) money besides      d) besides money
- 6) Rahul, Muralu, Srinivas and Arul are seated around a square table. Rahul is sitting to the left of Murali, Srinivas is sitting to the right of Arul. Which of the following pairs are seated opposite each other ? (2017 – EE)

